

PRICE
7/6

Practical Wireless

EVEREST TUNER

PUBLISHED BY GEO. NEWNES LTD., TOWER HOUSE, SOUTHAMPTON STREET, LONDON W.C.2.

BLUEPRINT
6

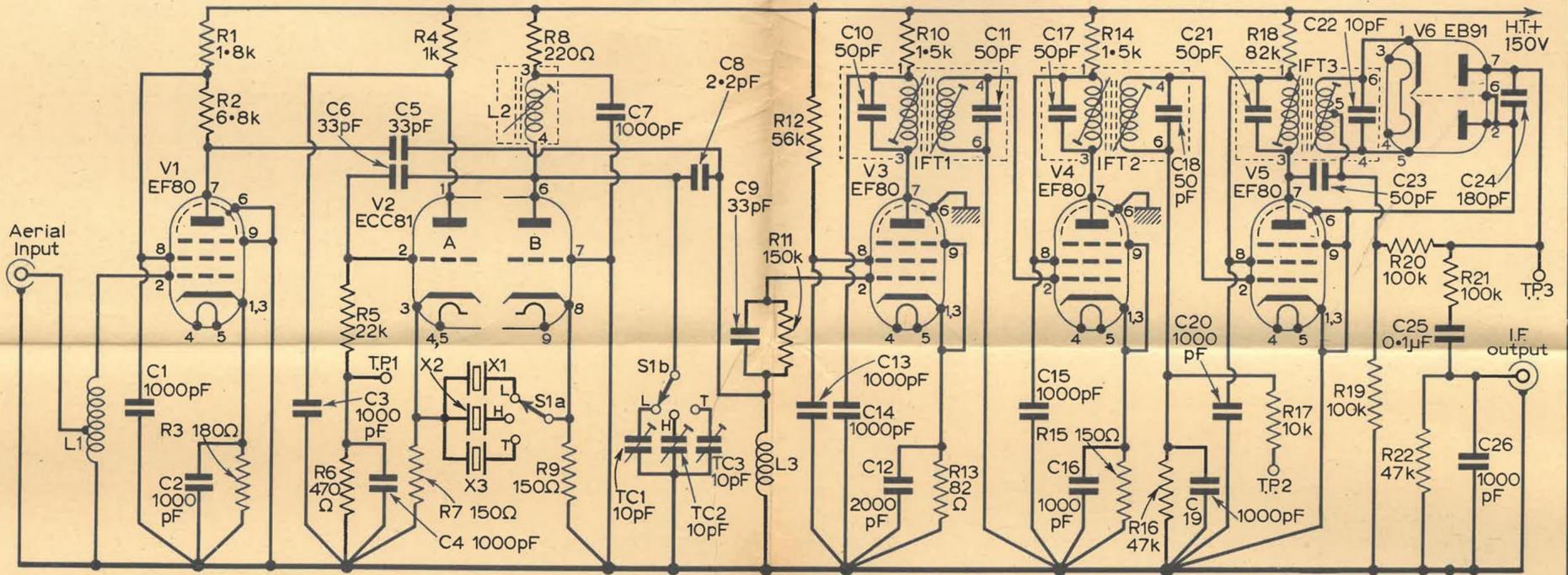


Fig. 1 - The circuit diagram.

For switch wiring see Fig. 5

Tags marked 'MC' denote earthing connections to chassis

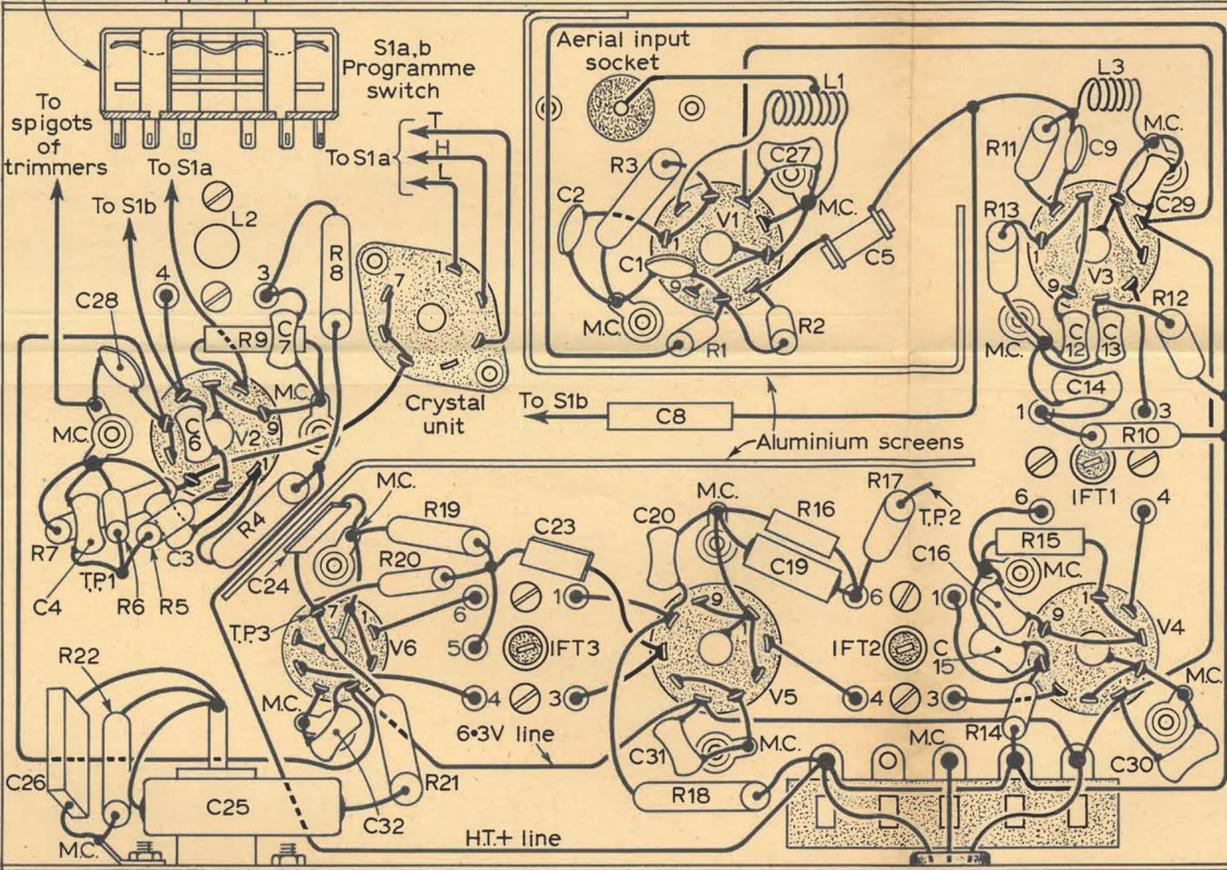


Fig. 2 - The underchassis wiring diagram.

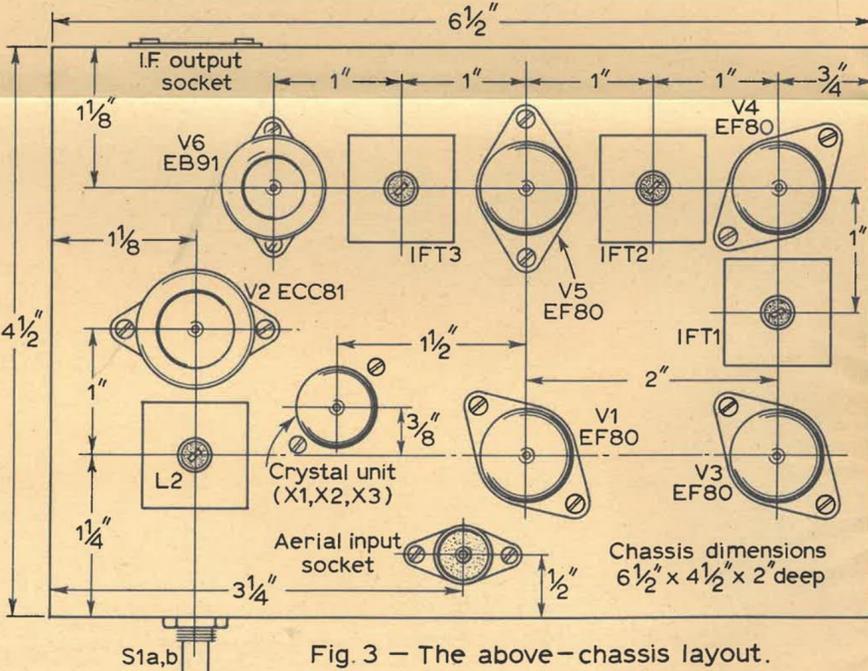


Fig. 3 - The above-chassis layout.

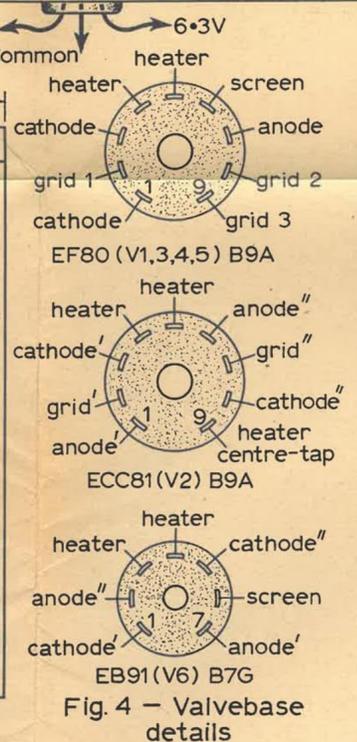


Fig. 4 - Valvebase details

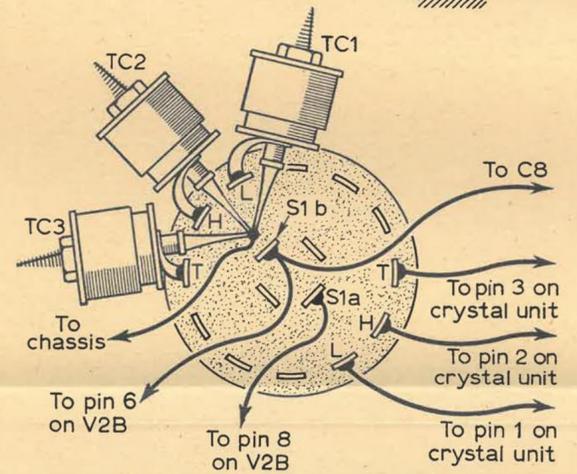


Fig. 5 - Programme-switch wiring.

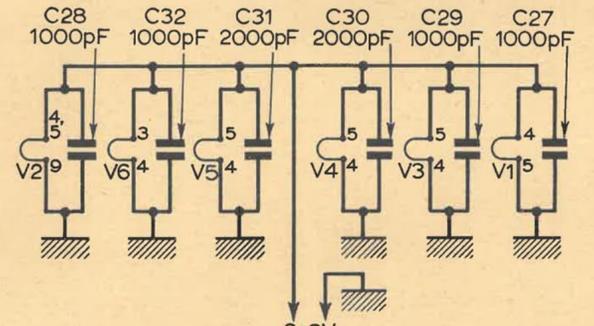


Fig. 6 - Heater circuit details.

COMPONENTS LIST

Resistors: (All 1/2W, 10% unless otherwise stated.)

R1 1.8k	R12 56k	C25 0.1µF paper 250VW
R2 6.8k	R13 82Ω	C26 1000pF 10% silver-mica
R3 180Ω	R14 1.5k	C27 1000pF ceramic
R4 1k	R15 150Ω	C28 1000pF ceramic
R5 22k	R16 47k	C29 1000pF ceramic
R6 470Ω	R17 10k	C30 2000pF ceramic
R7 150Ω	R18 82k	C31 2000pF ceramic
R8 220Ω	R19 100k*	C32 1000pF ceramic
R9 150Ω	R20 100k*	TC1, TC2, TC3 10pF bee-hive trimmers
R10 1.5k	R21 100k†	
R11 150k	R22 47k	

* Matched to 1% † see text

Capacitors:

C1 1000pF ceramic	C25 0.1µF paper 250VW
C2 1000pF ceramic	C26 1000pF 10% silver-mica
C3 1000pF ceramic	C27 1000pF ceramic
C4 1000pF ceramic	C28 1000pF ceramic
C5 33pF ceramic	C29 1000pF ceramic
C6 33pF ceramic	C30 2000pF ceramic
C7 1000pF ceramic	C31 2000pF ceramic
C8 2.2pF ceramic	C32 1000pF ceramic
C9 33pF ceramic	
C10 50pF 1% min. silver-mica	
C11 50pF 1% min. silver-mica	
C12 2000pF ceramic	
C13 1000pF ceramic	
C14 1000pF ceramic	
C15 1000pF ceramic	
C16 1000pF ceramic	
C17 50pF 1% min. silver-mica	
C18 50pF 1% min. silver-mica	
C19 1000pF ceramic	
C20 1000pF ceramic	
C21 50pF 1% min. silver-mica	
C22 10pF ±1pF min. silver-mica	
C23 50pF 1% min. silver-mica	
C24 180pF 10% silver-mica	

Coils: L1, L2 see text

I.F. Transformers: For winding details, see text

Valves (Mullard): V1 EF80, V2 ECC81, V3 EF80, V4 EF80, V5 EF80, V6 EB91

Crystal Unit (Brimar): See text

Coil Formers etc. (Aladdin): Four 2 1/2in. formers, cans, eye-letted paxolin wafers and eight dust cores

Chassis (aluminium): About 6 1/2in. x 4 1/2in. x 2in. (see text)

Programme Switch: 4-pole, 3-way

Miscellaneous: Five B9A valveholders (all with skirts; one with can, for ECC81); two B7G valveholders (one with skirt and can); aluminium sheet for under-chassis screens (see text); connecting wire, sleeving and wire for coil winding (see text); tag-strip; two coaxial sockets; etc.