
PRESENTED FREE WITH "PRACTICAL WIRELESS" NOVEMBER 1962


**Practical Wireless** 


## R PRE-AMPLIFIER

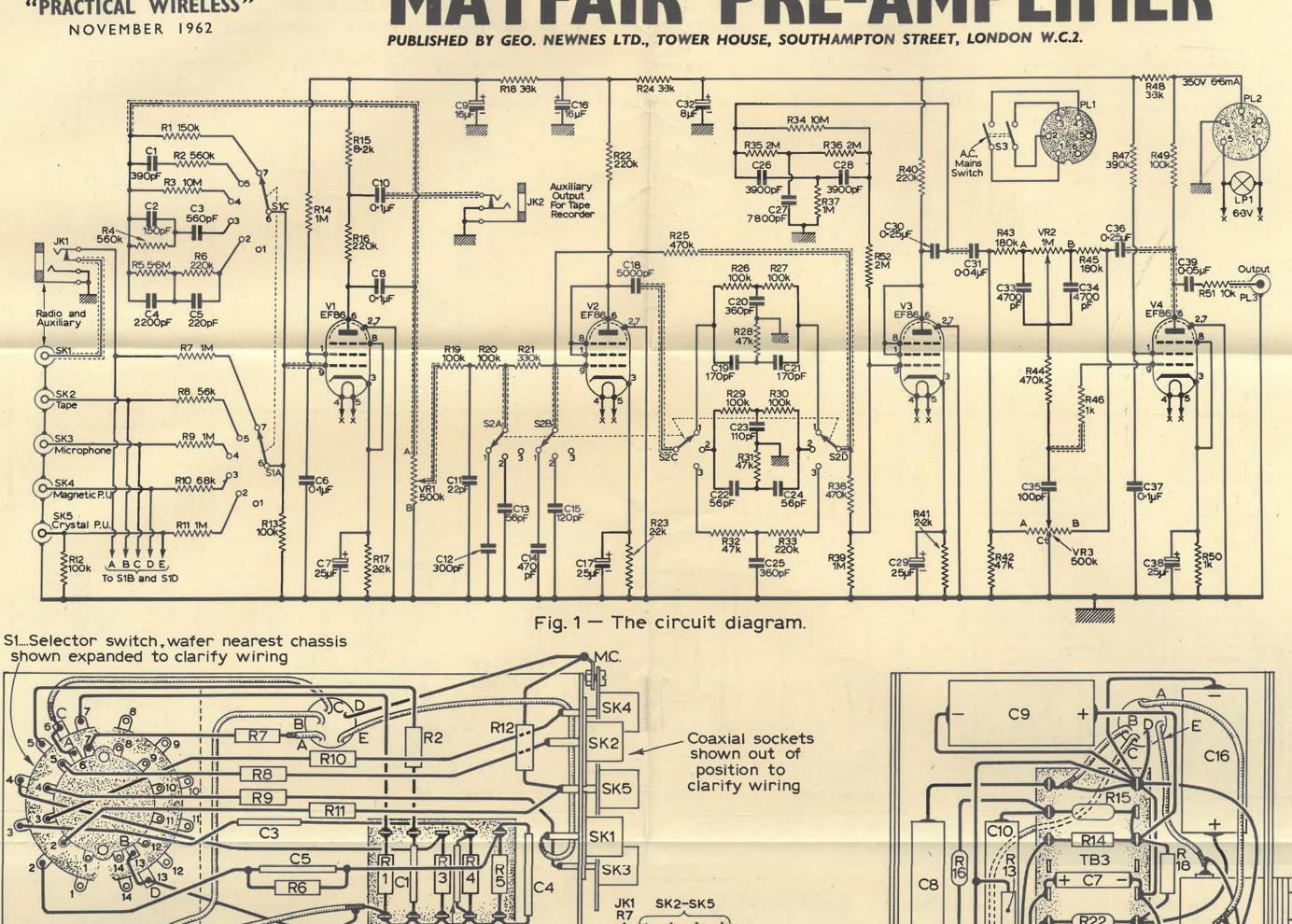


TB1 VR1 AB Volume TB2 **EF86** Treble Filter V2 EF86 V3 EF86 R26 R28 C33 C'21 Bass VR2 V4 EF86 M.C. C36 C31 VR3 Treble Front panel shown laid flat to clarify wiring

Fig. 2 - Above chassis wiring.

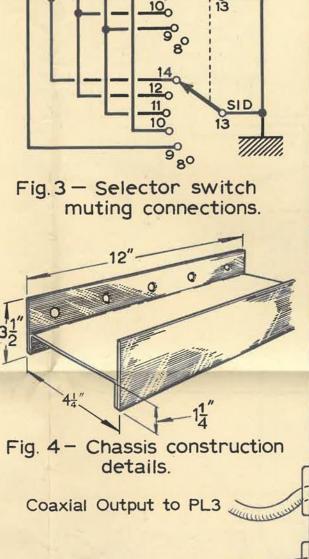

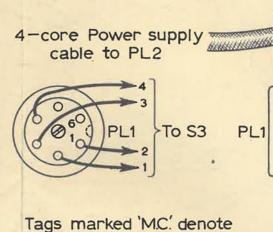

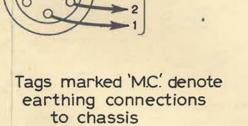

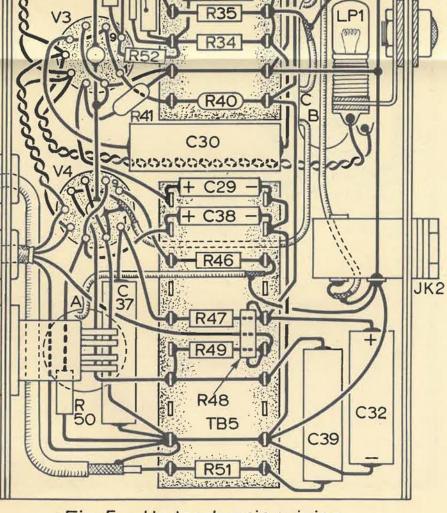


Fig. 5 - Underchassis wiring.