# PERFORMANCE ANALYSIS OF 3- AND 4-COIL FM TUNERS\* USING RCA HIGH-FREQUENCY TRANSISTORS

by


R. V. Fournier, C. H. Lee, and R. T. Peterson Radio Corporation of America Electronic Components and Devices Somerville, N.J.

High-quality FM multiplex performance imposes stringent requirements on tuner gain, quieting, and limiting sensitivities. In addition, the spurious response of the tuner becomes relatively more im-

The selectivity of the antenna and rf interstage coils is shown in Fig.2, together with the in-circuit unloaded and loaded coil Q's used to obtain the desired selectivity and the over-all response of the

portant as the receiver sensitivity is increased. When high-performance receivers are used in metropolitan areas, good receiver operation is made very difficult (if not impossible, in some instances) by the presence of powerful stations which transmit frequencies close to the carrier, image, or half-if frequency of the desired carrier. When harmonics of other signals combine with harmonics of the receiver, sum or difference frequencies close to the intermediate frequency may produce an undesired response.

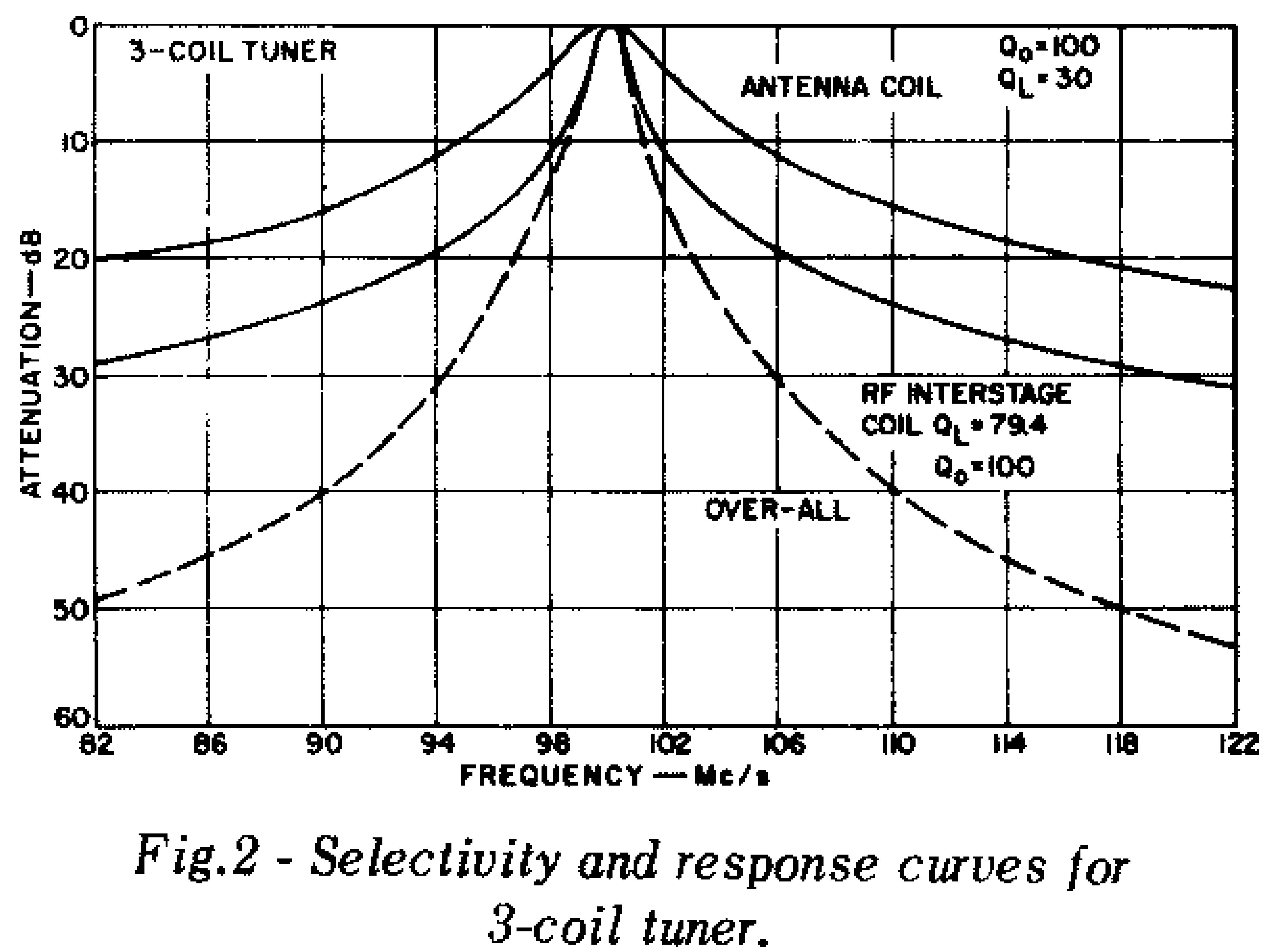This paper describes a design analysis program undertaken to improve the spurious-response immunity of high-quality tuners. Commercially available 3-and 4-coil tuners were investigated thoroughly to determine the quiescent operating points, circuit configurations, and component layouts which would provide maximum tuner sensitivity while maintaining good tuner gain and low noise.




# **3-COLL TUNER PERFORMANCE**

tuner. The tuner was assembled carefully to assure that component layout and/or ground loops did not alter the degree of loading necessary to obtain the


The signal-to-noise ratio and limiting performance of the tuner as a function of input signal level from a 75-ohm source generator are shown in oscillator signals (see Appendix B) that were as Fig.3. For these measurements, the tuner was connected to a 3-stage neutralized if amplifier that

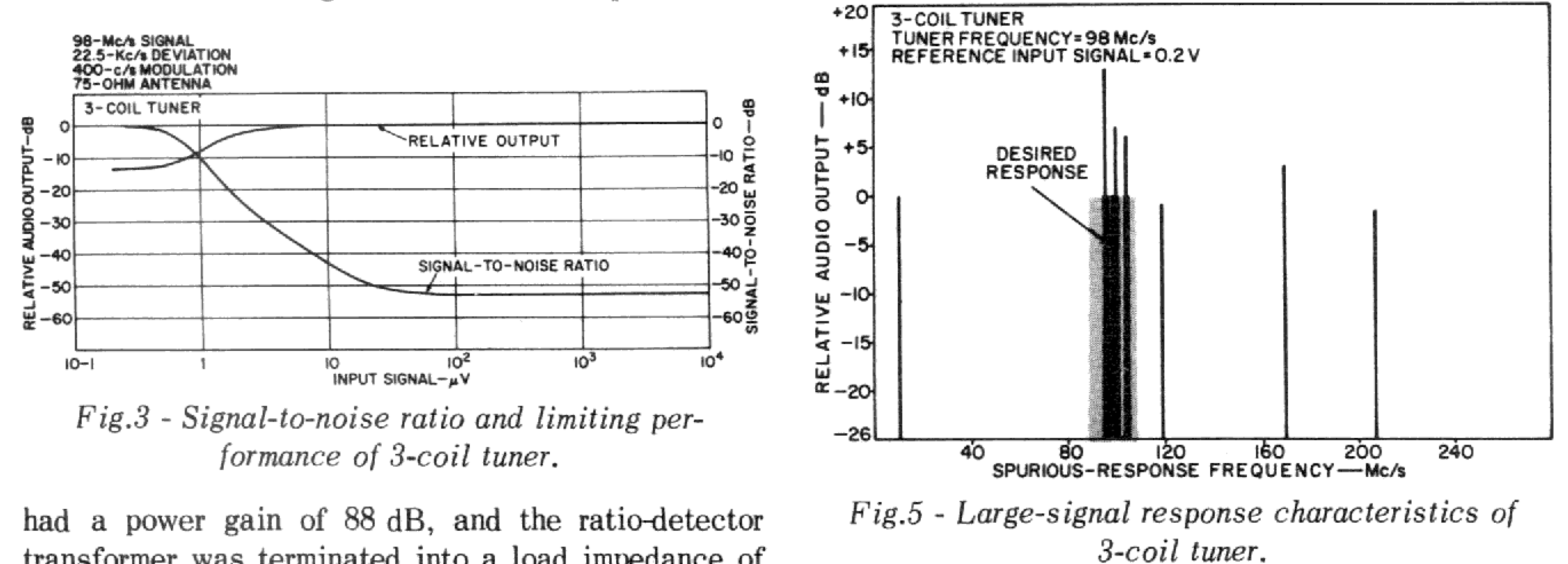much as 10 times the carrier deviation indicated the presence of harmonics of either the incoming rf or high as the 10th order of magnitude.



transformer was terminated into a load impedance of 10,000 ohms.

Fig.4 shows small-signal response characteristics of the tuner at the 20-dB quieting-sensitivity input level of 1.6 microvolts. Although the use of a pi-section tunable trap (such as that used with permeability tuners, see Appendix A) might provide

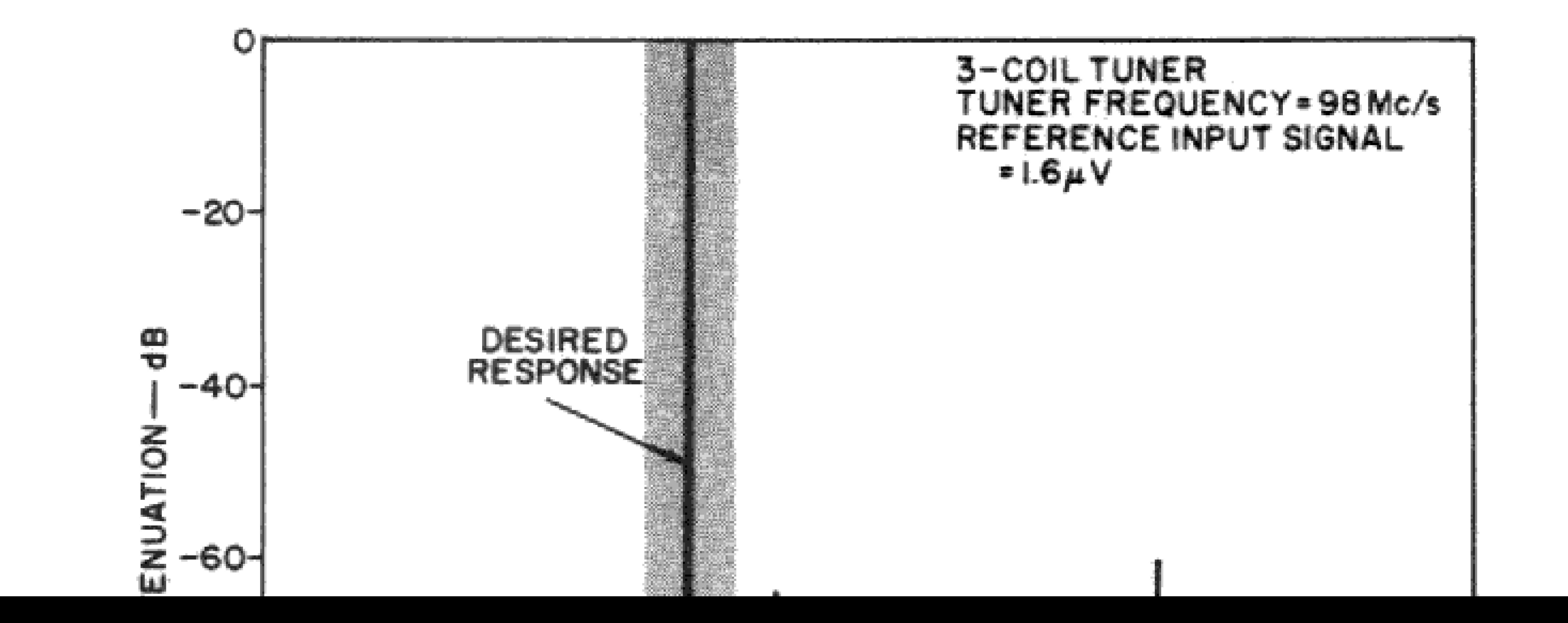

The most significant reduction in spurious counts across the band was obtained by modifications in three areas: (1) the oscillator circuit, (2) injection levels, (3) lead dress and component layout.

**Oscillator Circuit** - Investigations showed that the spurious-response characteristics of the tuner were improved when an external oscillator having a guaranteed harmonic suppression of at least 40 dB below its fundamental waveform was used. An oscillator circuit was developed which minimized the harmonic content of the waveform and eliminated any tendency toward parasitic oscillations in the circuit.

### 4-COIL TUNER PERFORMANCE

The circuit diagram of the 4-coil tuner is shown in Fig.6. As in the case of the 3-coil tuner, the common-emitter configuration was employed in the rf-amplifier and mixer stages, and the common-base configuration in the oscillator stage. The antenna Curves showing signal-to-noise ratio and relative receiver output as a function of input signal levels are shown in Fig.8. Because of the additional coupling loss in the double-tuned antenna, the noise quieting and limiting sensitivities are reduced by approximately 4 dB.


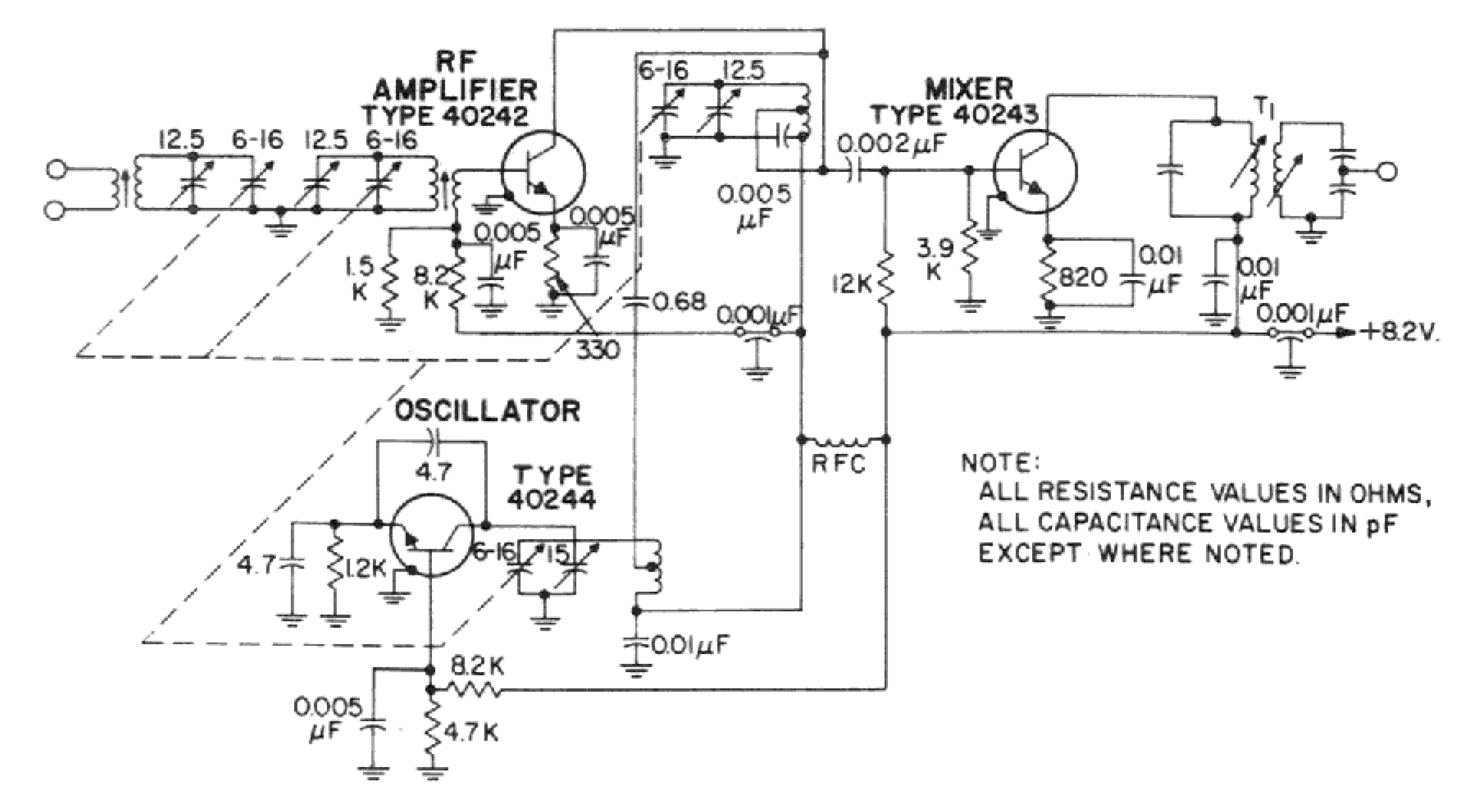


Fig.6 - Circuit diagram of 4-coil FM tuner.

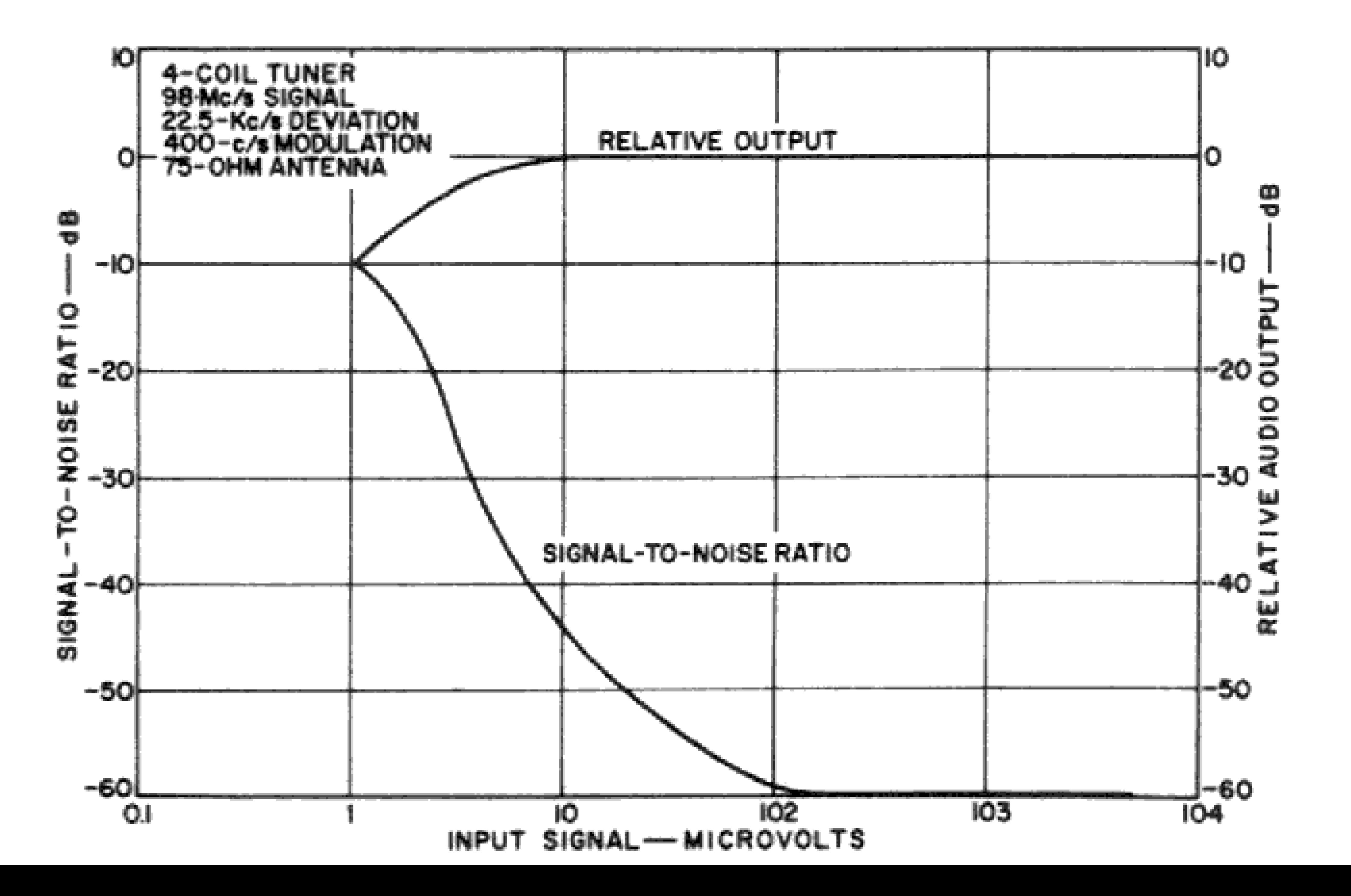circuit was double-tuned instead of the rf interstage coils to obtain good selectivity ahead of the rfamplifier stage and thus minimize its contribution to harmonic generation. The resulting coupling loss, plus mismatch loss in the antenna, degrades the signal-to-noise performance of the tuner by approximately 4 dB.



The selectivity curves for the double-tuned antenna and the single-tuned rf interstage coils and the over-all response curve for the tuner are shown in Fig.7. The over-all selectivity curve shows

this figure with that for the 3-coil tuner (Fig.4) readily shows the effectiveness of the double-tuned antenna. The half-if response is noticeably absent in Fig.9. In fact, the only measurable response within the FM band occurred at 106.9 megacycles per second, which is 8.9 megacycles per second on the high side of the carrier, and was 98 dB below the reference signal.


The large-signal response of the 4-coil tuner receiver is shown in Fig.10. It can be seen that even on large signals there is no half-if response

+25	
	4-COIL TUNER
+204	TUNER FREQUENCY = 98 Mc/s REFERENCE INPUT SIGNAL = 0.2 V
<u>an</u>	
0 + 15	REFERENCE INFUT SIGNAL = 0.2 V

## TABLEI

# COMPARISON OF TUNER PERFORMANCE CHAR-ACTERISTICS MEASURED AT 98 Mc/s WITH AN UNBALANCED INPUT OF 75 OHMS

Sensitivity:	3-coil tuner	4-coil tuner		
For 20-dB quieting	1.6	2.5	$\iota V$	
For 30-dB quieting	3.2	3.5	$\mu v$	
For -3-dB limiting	1.6	3.2	μV	
Rejection:				
IF (10.7 Mc/s)	97	93	dB	
1/2-IF (103.35 Mc/s)	76	103	dB	
Image (119.4 Mc/s)	64	82	dB	
Double 1/2-IF				
(206.7 Mc/s)	60	88	dB	
IF amplifier gain	88	88	dB	
Over-all receiver band-				
width	<b>290</b>	270	kc/s	
Field test results in metropolitan areas (installed in auto with				
30" antenna)	Fair to Goo	d Very Goo	d	

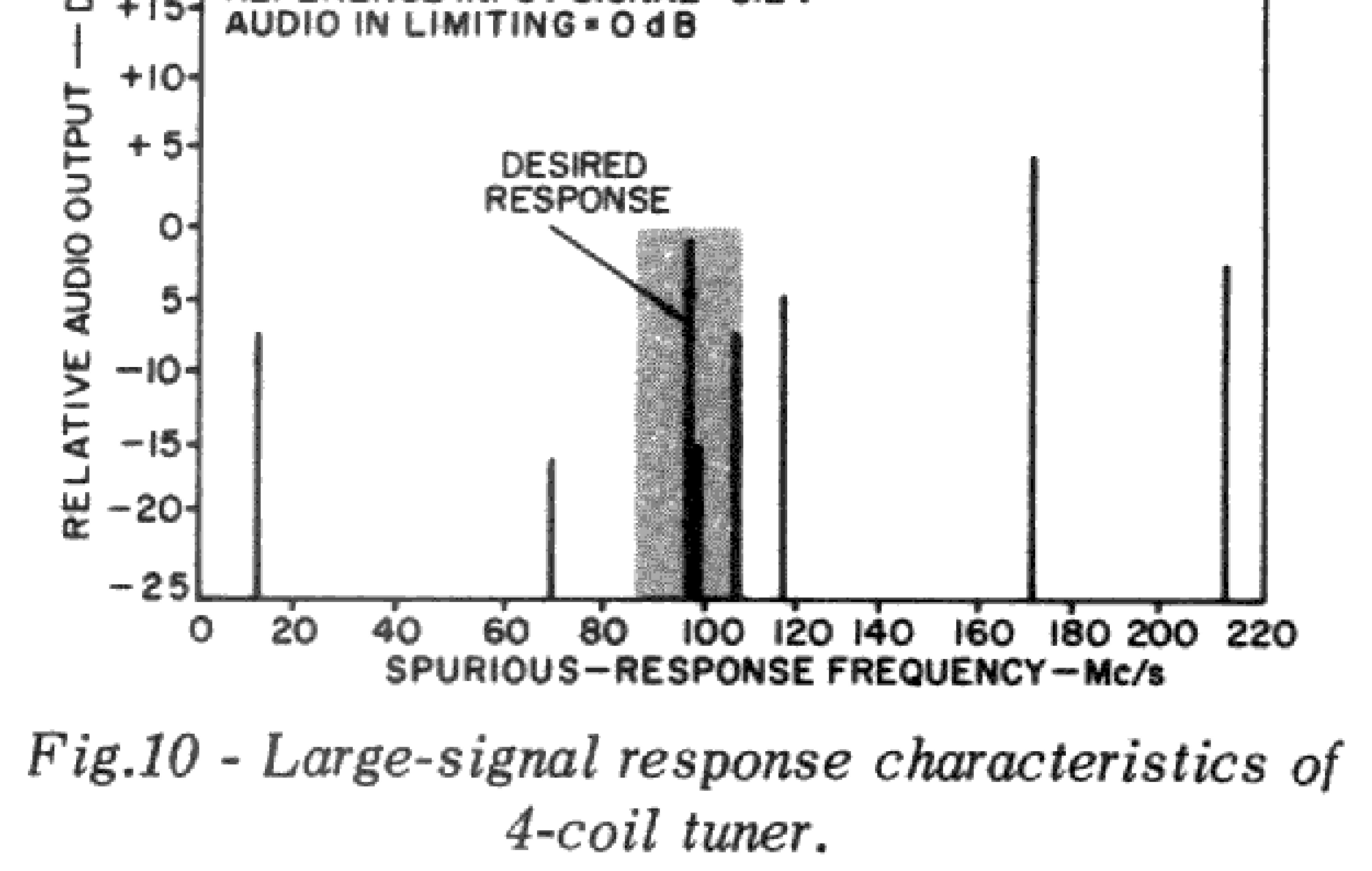

to the tuner. Only two responses occurred in the FM band, with audio output levels 14.5 dB below the reference at 98.7 megacycles per second and 6 dB below the reference at 106.9 megacycles per second.

instances, it was possible to hear three different stations simultaneously when the standard, commercial 3-coil tuner was used. When the modified 3-coil tuner shown in Fig.1 was used, immunity from spurious responses was generally good, although a strong carrier transmitting on a frequency 6.4 megacycles per second on the high side of the tuned frequency caused appreciable interference. When the 4-coil tuner was used, only a "tick" was heard

### SUMMARY

Table I compares the receiver measurements for the 3- and 4-coil tuners. Although the coupling loss introduced by the double-tuned antenna in the

tests, supplemented by extensive field testing, have will shown that the 4-coil tuner provides acceptable performance in areas where even the best 3-coil tuners provide only marginal performance.

# APPENDIX A

The use of a pi-section tunable-trap rf interstage coil is well suited to permeability tuners in which the coils may be electrically isolated from ground. In the case of capacitive tuning, the use of a pisection tunable trap requires that one section of the tuning gang be electrically isolated from the other sections. For practical reasons, only parallel capacitive tuning was evaluated in the investigation described. However, the calculations below illustrate the difference in attenuation between a paralleltuned circuit and a pi-section circuit.

here 
$$\overline{\underline{X}}$$
 is given by  
 $\overline{\underline{X}} = (Q_L^2 + f)/f_o$ 

For the half-if frequency of 103.35 megacycles per second,  $\rho$  is equal to 5.26, or 14.44 dB; at the image frequency of 119.4 megacycles per second,  $\rho$  is equal to 10.35, or 20.3 dB.

The equivalent circuit for a pi-section network with a tunable trap is shown in Fig.12(a). For the same parameters used in the case of the paralleltuned circuit (L = 0.224  $\mu$ H, A = 123.5 ohms, A' = 170 ohms) at an operating frequency f<sub>o</sub> of 98 megacycles per second and with the trap tuned to the image frequency of 119.4 megacycles per second, the pi-section circuit may be simplified as shown in Fig.12(b). The coil inductance and tuned resistance may then be transformed to the series combination by use of the following equations:

Fig.11 shows the equivalent circuit for a parallel-tuned circuit. As an illustrative example,

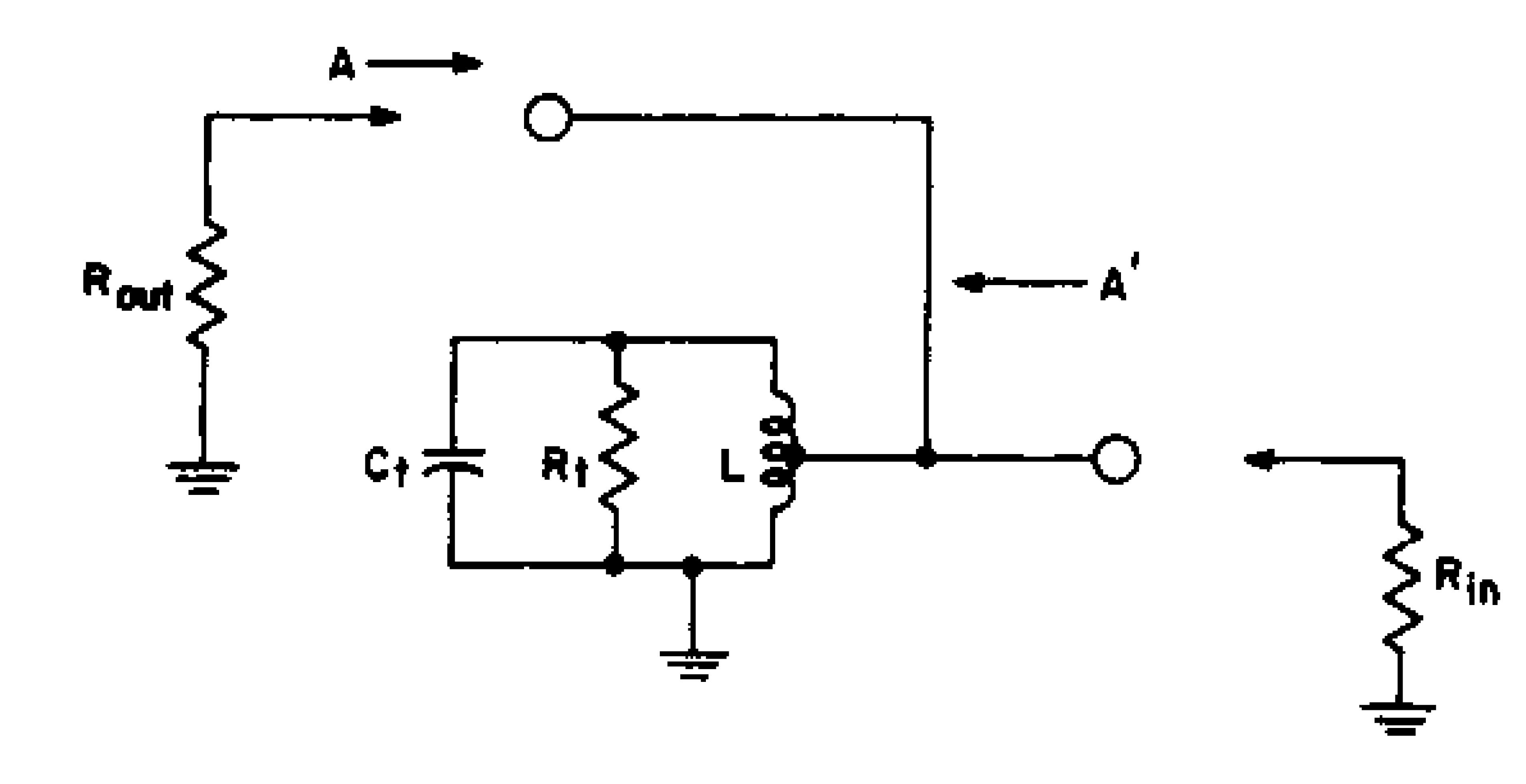



Fig.11 - Equivalent circuit for parallel-tuned circuit.

$$R_s = r_s / (1 - \alpha^2)^2$$
  
 $L_s = 1_s / (1 - \alpha^2)$ 

where  $R_s$  and  $L_s$  are the coil resistance and inductance, respectively, at the operating frequency  $f_o, r_s$  and  $l_s$  are the resistance and inductance values at the tuned frequency  $f_x$ , and  $\alpha$  is the ratio of operating frequency to tuned frequency  $f_x/f_o$ . The transformed circuit is shown in Fig.12(c). The circuit attenuation at the half-if frequency of 103.35 megacycles per second is 8.2 dB, and the attenuation at the image frequency of 119.4 megacycles per second is 36.48 dB.

the following parameter values are assumed for this circuit:

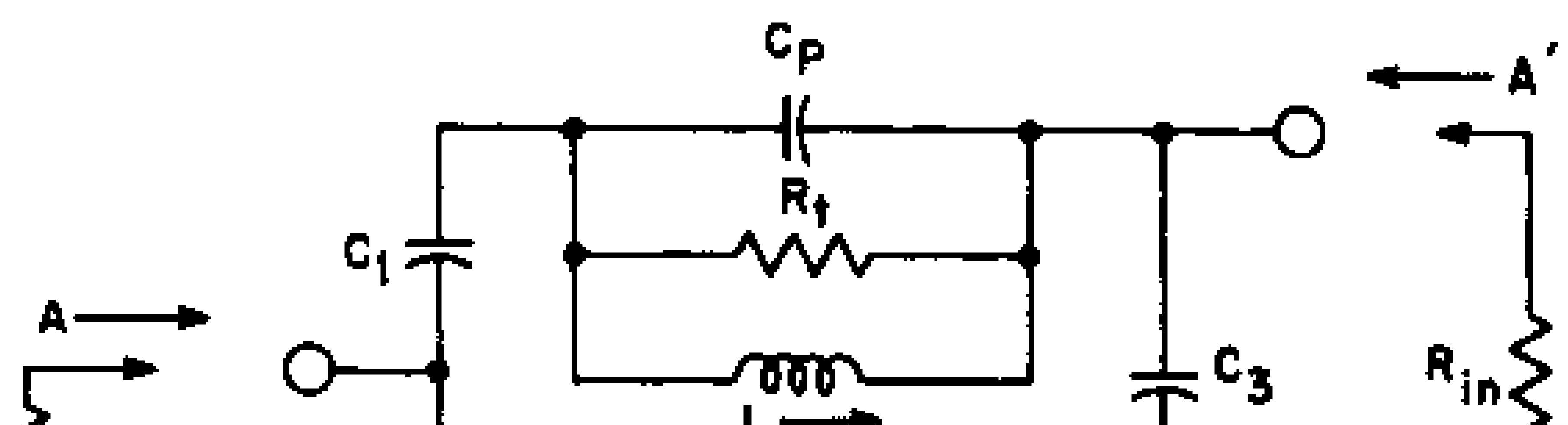operating frequency,  $f_o = 98$  megacycles per second



### APPENDIX B

The characteristic  $E_i I_c$  curves of a transistor nay be represented by the following power series:  $I_c = A_o + A_1 E_i + A_2 E_i^2 + A_3 E_i^3 + A_4 E_i^4 \dots$ where  $I_c$  is the collector current for the input voltage  $E_i$ . In the case of a transistor mixer stage operated in the common-base or common-emitter configuration, the input voltage  $E_i$  may be represented by

 $\mathbf{E}_{\mathbf{i}} = \mathbf{E}_{\mathbf{s}} \cos \omega_{\mathbf{s}} \mathbf{t} + \mathbf{E}_{\mathbf{h}} \cos \omega_{\mathbf{h}} \mathbf{t} - \mathbf{E}_{\mathbf{b}}$ 

where  $E_8 \cos \omega_8 t$  is the rf input voltage,  $E_h \cos \omega_h t$  is the local-oscillator input voltage, and  $E_b$  is the bias voltage.

where  $\omega_s = 2\pi f_s$  ( $f_s$  = angular frequency of the rf signal)

- $\omega_{h} = 2\pi f_{h}$  ( $f_{h} = angular$  frequency of the oscillator signal)
- $\omega_{sn} = 2\pi f_{sn}$  (f<sub>sn</sub> = harmonics of the signal frequency)
- $\omega_{hn} = 2\pi f_{hn}$  ( $f_{hn}$  = harmonics of the oscillator frequency)
- n = number of the harmonic frequency  $(1, 2, 3, \ldots)$

These difference-frequency equations show that harmonics of either the rf or the oscillator frequency

These two equations can be combined to provide an expression for the conversion transconductance of the mixer in which the difference-frequency outputvoltage terms  $E_{if}$  may be represented by

 $E_{if} = A E_s E_h^n \cos (n \omega_s - \omega_{hn})$  $E_{if} = A E_s^n E_h \cos (n \omega_h - \omega_{sn})$ 

may produce an undesired signal equal to the intermediate frequency of the receiver. Furthermore, because the interfering signal involves signalfrequency harmonics, the frequency deviation is increased. As a result, it is possible that a spurious response may cause an audio output greater than that produced by the desired carrier.

### REFERENCES

- (1) M. J. O. Strutt, "On Conversion Detectors", Proc. I.R.E., vol. 22, P. 981, August 1934.
- (2) K.R. Starley, Radio Receiver Design, Part 1, Chapman and Hall Ltd, London.
- (3) RCA Application Note, AN-185, "Modulator and Converter Circuits Using the RCA - 7360 Beam-Deflection Tube", 1960.

The attached RCA paper provides a simple "worked example" of the benefits of extra front-end selectivity for FM receivers.

That showed that in the case of bipolar transistors, it was better to place the bandpass at the input and sacrifice some noise performance in favour of better spurious response rejection. When dual-gate mosfets arrived, it was more common to place the bandpass at the interstage, with a single-stage at the input. Presumably the better inherent linearity of the mosfets allowed this. Although there were some mosfet examples with a bandpass input, such as the D&W four-gang front ends (<u>https://vintage-radio.net/forum/showthread.php?p=1153245</u>).

Cheers,